

Chapter 4

Bipolar Junction Transistors. Home Work Solutions

4.1 Problem 4.33

A single measurement indicates the emitter voltage of the transistor in the circuit of Figure (4.1) to be 1.0 V. Under the assumption that $|V_{BE}| = 0.7 \text{ V}$, what are $V_B, I_B, I_E, I_C, V_C, \beta$ and α ?

Solution

The emitter current I_E is given by:

$$\begin{aligned} I_E &= \frac{V_{EE} - V_E}{R_E} \\ &= \frac{5 - 1}{5 \times 10^3} \\ &= 0.8 \text{ mA} \end{aligned}$$

The base voltage V_B is given by:

$$\begin{aligned} V_B &= V_E - V_{BE} \\ &= 1.0 - 0.7 \\ &= 0.3 \text{ V} \end{aligned}$$

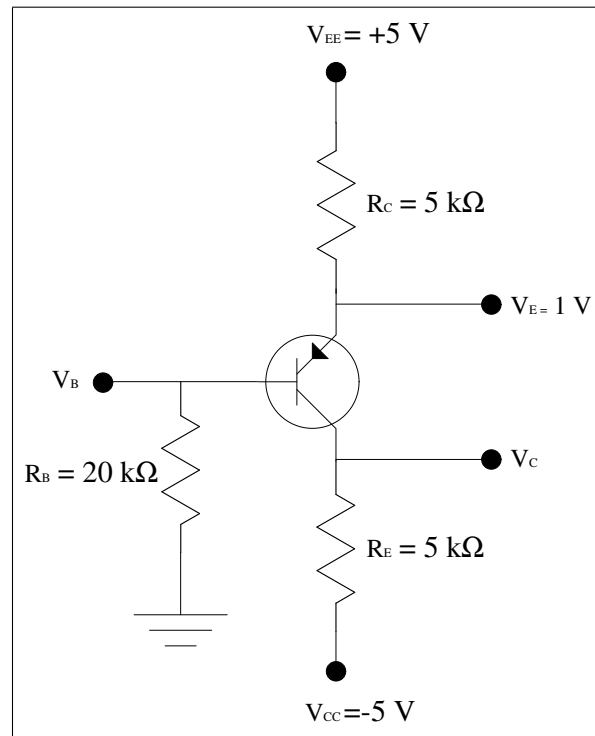


Figure 4.1:

The base current I_B is:

$$\begin{aligned}
 I_B &= \frac{V_B}{R_B} \\
 &= \frac{0.3}{20 \times 10^3} \\
 &= 15\ \mu\text{A}
 \end{aligned}$$

The collector current I_C is given by;

$$\begin{aligned}
 I_C &= I_E - I_B \\
 &= 0.8 - 0.15 \\
 &= 0.785\text{ mA}
 \end{aligned}$$

The collector voltage V_C is given by:

$$\begin{aligned}
 V_C &= V_{CC} + I_C R_C \\
 &= -5 + 0.785 \times 5 \\
 &= -1.075\text{ V}
 \end{aligned}$$

Now the transistor β is:

$$\begin{aligned}\beta &= \frac{I_C}{I_B} \\ &= \frac{0.785}{0.015} \\ &= 52.3\end{aligned}$$

Finally, the transistor α is given by:

$$\begin{aligned}\alpha &= \frac{I_C}{I_E} \\ &= \frac{0.785}{0.8} \\ &= 0.98\end{aligned}$$

4.2 Problem 4.46

For reasonably linear small signal operation of a BJT, v_{be} must be limited to no larger than 10 mV. To what percentage change of bias current does this correspond? For a design in which the required output voltage signal is 10 mA peak, what bias current required? What is the corresponding value of g_m ?

Solution

The total (ac and dc) collector current i_C is:

$$\begin{aligned}i_C &= I_C e^{v_{be}/V_T} \\ &= I_C + i_c \\ \frac{i_c}{I_C} &= e^{v_{be}/V_T} - 1\end{aligned}$$

Taking $v_{be} = 10$ mV and $V_T = 25$ mV, we get:

$$\begin{aligned}\frac{i_c}{I_C} &= e^{10/25} - 1 \\ &= 0.492 \\ &= 49.2\%\end{aligned}$$

For $i_c = 10$ mA while $v_{be} = 10$ mV, we get:

$$\begin{aligned}I_C &= \frac{10}{0.492} \\ &= 20.3 \text{ mA}\end{aligned}$$

Finally, for $I_C = 20.3$ mA, g_m is:

$$\begin{aligned}g_m &= \frac{I_C}{V_T} \\ &= \frac{20.3}{25} \\ &= 0.81 \text{ A/V}\end{aligned}$$

4.3 Problem 4.48

For the circuit of Figure (4.2), V_{BE} is adjusted so that $V_C = 2$ V. If $V_{CC} = 10$ V, $R_C = 2$ k Ω , and a signal $v_{be} = 0.004 \sin \omega t$ volts is applied, find expressions for the total instantaneous quantities $i_C(t)$, $v_C(t)$, and $i_B(t)$. The transistor has $\beta = 100$. What is the voltage gain.

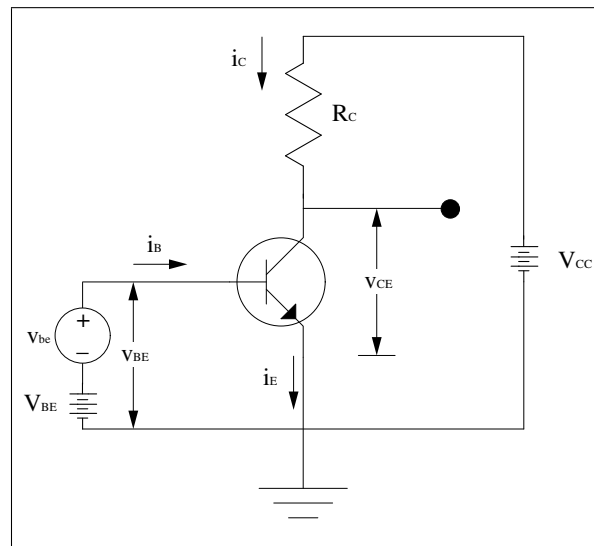


Figure 4.2:

Solution

Using the given values of V_C of 2 V, V_{CC} of 10 V, and R_C of 2 k Ω , the collector current is:

$$\begin{aligned}
 I_C &= \frac{V_{CC} - V_C}{R_C} \\
 &= \frac{10 - 2}{2 \times 10^3} \\
 &= 4 \text{ mA}
 \end{aligned}$$

Using the the T-model equivalent circuit, the total collector current is:

$$\begin{aligned}i_C(t) &= I_C + g_m v_{be} \\g_m &= \frac{I_C}{V_T} \\i_C(t) &= I_C + \frac{I_C}{V_T} v_{be} \\v_{be}(t) &= 0.004 \sin \omega t \\i_C(t) &= I_C + \frac{I_C}{V_T} \times \sin \omega t \\&= 4 + \frac{4}{2.5 \times 10^4} \times 0.004 \sin \omega t \\&= 4 + 0.64 \sin \omega t \text{ mA}\end{aligned}$$

The total collector voltage $v_C(t)$ is:

$$\begin{aligned}v_C(t) &= V_{CC} - R_C i_C(t) \\&= 10 - 2 \times 10^3 \times (4 \times 10^{-3} + 0.64 \times 10^{-3} \sin \omega t) \\&= 2 - 1.28 \sin \omega t \text{ V}\end{aligned}$$

The total base current $i_B(t)$ is:

$$\begin{aligned}i_B(t) &= \frac{i_C(t)}{\beta} \\&= \frac{4 + 0.64 \sin \omega t}{100} \\&= 0.04 + 0.0064 \sin \omega t \text{ mA} \\&= 40 + 6.4 \sin \omega t \text{ }\mu\text{A}\end{aligned}$$

The peak value of the the ac-component of output voltage v_c is 1.28 V and the peak value of the input is 0.004 V, the voltage gain is then given by:

$$\begin{aligned}A_v &= -\frac{1.28}{0.004} \\&= -320\end{aligned}$$

4.4 Problem 4.67

Sketch the $i_C - v_{CE}$ characteristics of an npn transistor having $\beta = 100$ and $V_A = 100$ V. Sketch characteristic curves for $i_B = 20, 50, 80,$ and $100 \mu\text{A}$. For the purpose of this sketch, assume that $i_C = \beta i_B$ at $v_{ce} = 0$. Also sketch the load line obtained for $V_{CC} = 10$ V and $R_C = 1k\Omega$. If the dc bias current into the base is $50 \mu\text{A}$, write the equation for the corresponding $i_C - v_{CE}$ curve. Also, write the equation for the load line, and solve the two equations to obtain V_{CE} and I_C . If the input signal causes a sinusoidal signal of $30\text{-}\mu\text{A}$ peak amplitude to be superimposed on I_B , find the corresponding signal components of i_C and v_{CE} .

Solution

the equation for the characteristic $v_{CE} - i_C$ is given by:

$$i_C = m v_{CE} + C$$

where m is the slope of the line and C is the y-intercept. We are given the the y-intercept as βi_B and the x-intercept as $V_A = 100$ V. The slope m can then be determined from the two intercepts as:

$$\begin{aligned} m &= \frac{C}{V_A} \\ &= \frac{\beta i_B}{100} \end{aligned}$$

So, the slopes m_1 of line 1, m_2 of line 2, m_3 of line 3, and m_4 of line 4 are 0.02, 0.05, 0.08, and 0.1 respectively. While the y-intercepts are 2, 5, 8, and 10 mA respectively. Of course all lines should meet at the x-intercept of -100 V. Using this information one then can plot the $v_{CE} - i_C$ characteristics for the four given base currents. The load line has a x-intercept of V_{CC} and a slope of $-1/R_C$, so in the graph it connects the points with coordinates of $(V_{CC}, 0)$ and $(0, V_{CC}/R_C)$ i.e. (10 V, 0) and (0, 10 mA). The four characteristic curves and the load line are shown in Figure (4.3).

The equation for the line with a base current $i_B = 50 \mu\text{A}$ is:

$$\begin{aligned} i_C &= \beta i_B + \frac{\beta i_B}{V_A} v_{CE} \\ &= 5 + 0.05 v_{CE} \quad \text{mA} \end{aligned} \tag{4.1}$$

The load line equation is:

$$\begin{aligned} V_{CC} &= i_C R_C + v_{CE} \\ i_C &= \frac{V_{CC} - v_{CE}}{R_C} \\ &= 10 - v_{CE} \quad \text{mA} \end{aligned} \tag{4.2}$$

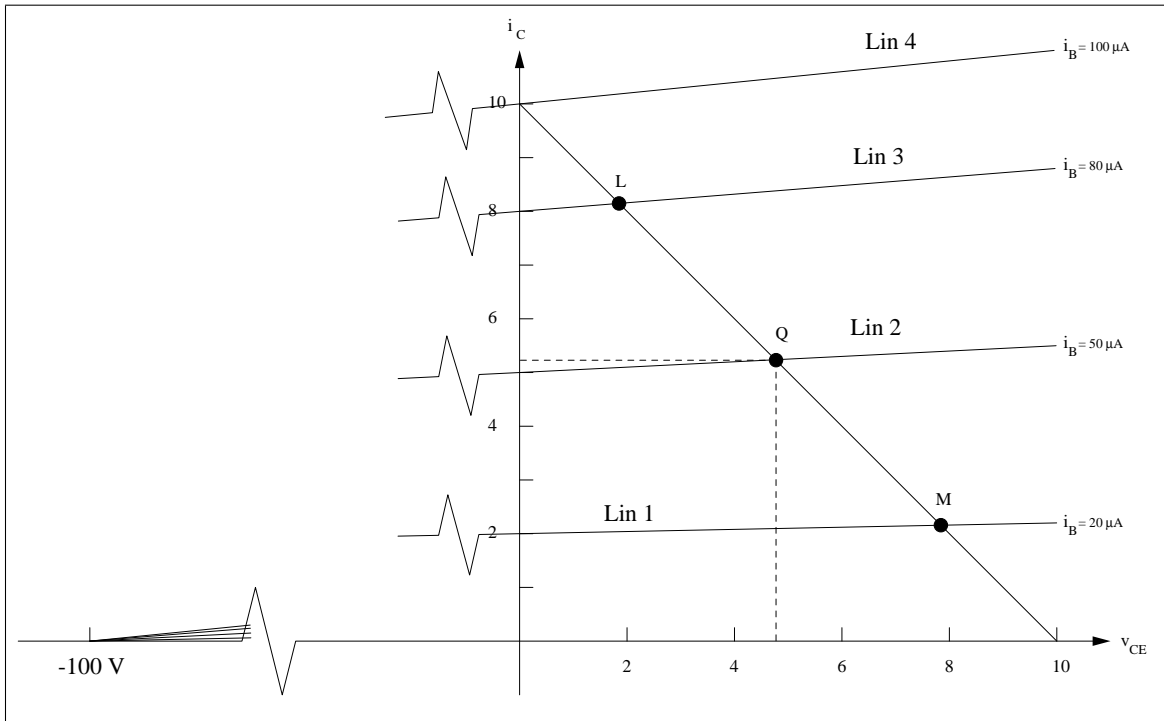


Figure 4.3:

Solving Equations (4.1) and (4.2) provides the intersection of the line for $i_B = 50 \mu\text{A}$ and the load line, i.e. the dc bias point Q with coordinates (V_{CE}, I_C) . The solution is:

$$I_C = 5.24 \text{ mA}$$

and

$$V_{CE} = 4.76 \text{ V}$$

When a signal of $30 \mu\text{A}$ is superimposed on $I_B = 50 \mu\text{A}$, the operating point moves along the load line between point L ($I_B = 80 \mu\text{A}$) and point M ($I_B = 20 \mu\text{A}$). To find the coordinates of point L we solve the load line equation Equation (4.2) and Line 3 equation given by:

$$i_C = 8 + 0.08 v_{CE}$$

the solution gives:

$$\begin{aligned} i_C|_L &= 8.15 \text{ mA} \\ v_{CE}|_L &= 1.85 \text{ V} \end{aligned}$$

Similarly we can find the coordinates of point M to be:

$$\begin{aligned} i_C|_M &= 2.16 \text{ mA} \\ v_{CE}|_M &= 7.84 \text{ V} \end{aligned}$$

The ac output current signal is zero at point Q and will have a positive peak \hat{i}_{c+} at point L and a negative peak \hat{i}_{c-} at point M where:

$$\begin{aligned}\hat{i}_{c+} &= i_C|_L - I_C \\ &= 8.15 - 5.24 \\ &= 2.91 \text{ mA} \\ \hat{i}_{c-} &= I_C - i_C|_M \\ &= 5.24 - 2.16 \\ &= 3.08 \text{ mA}\end{aligned}$$

and the peak-peak current is 5.99 mA. Similarly one can calculate the voltage of the output signal as:

$$\begin{aligned}\hat{v}_{ce+} &= v_{CE}|_L - V_{CE} \\ &= 7.84 - 4.76 \\ &= 3.08 \text{ V} \\ \hat{v}_{ce-} &= V_{CE} - v_{CE}|_M \\ &= 4.76 - 1.85 \\ &= 2.91 \text{ mA}\end{aligned}$$

and the peak-peak voltage is 5.99 V. The output ac voltage (in volts) and the output ac current (in mA) are equal in magnitude because the slope of the load line is $(-1/1k\Omega)$.

4.5 Problem 4.78

For the common emitter amplifier shown in Figure (4.4), let $V_{CC} = 9\text{ V}$, $R_1 = 27\text{ k}\Omega$, $R_2 = 15\text{ k}\Omega$, $R_E = 1.2\text{ k}\Omega$, and $R_C = 2.2\text{ k}\Omega$. The transistor $\beta = 100$ and $V_A = 100\text{ V}$. Calculate the dc bias current I_E . If the amplifier operates between a source for which $R_s = 10\text{ k}\Omega$ and a load of $2\text{ k}\Omega$, replace the transistor with its hybrid- π model, and find the values of R_i , the voltage gain v_o/v_s , and the current gain i_o/i_i .

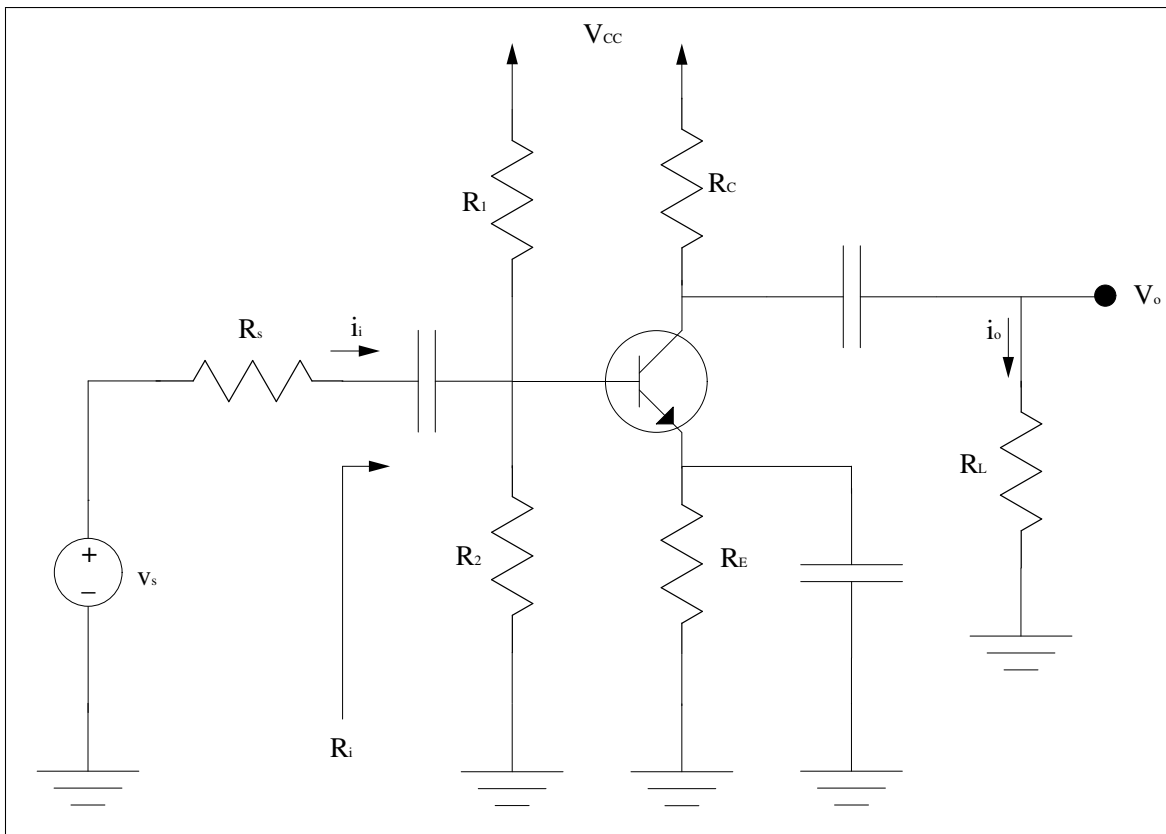


Figure 4.4: All capacitors are very large.

Solution

The hybrid- π model of the circuit is shown in Figure (4.5). the dc emitter current I_E is given by:

$$I_E = \frac{V_{BB} - V_{BE}}{R_E + \frac{R_B}{\beta+1}}$$

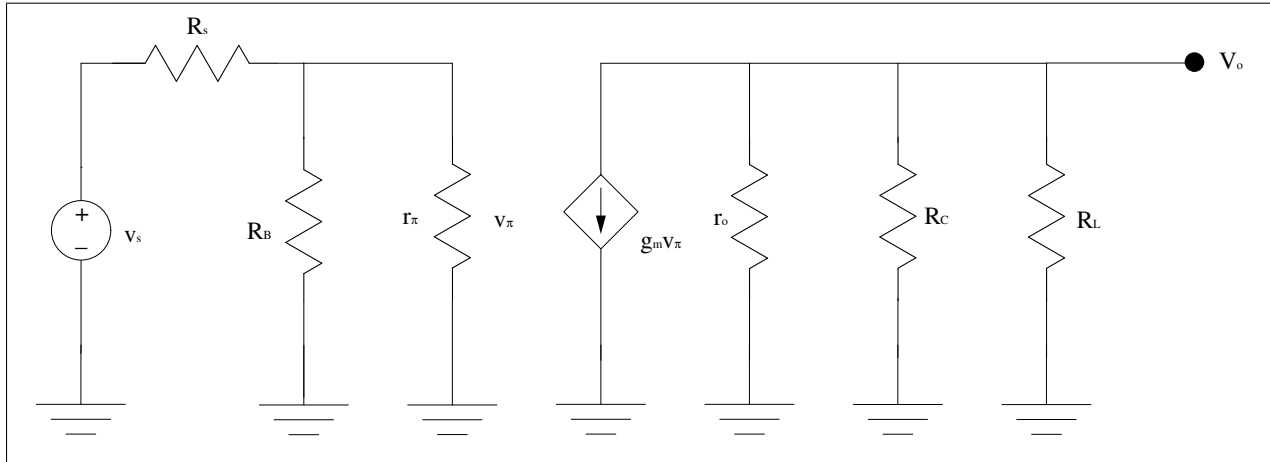


Figure 4.5: The hybrid- π -model of the circuit shown in Figure (4.4). $R_B = R_1 // R_2$.

where:

$$\begin{aligned}
 V_{BB} &= V_{CC} \times \frac{R_2}{R_1 + R_2} \\
 &= 9 \times \frac{15}{27 + 15} \\
 &= 3.21 \text{ V} \\
 &= 1.3 \text{ k}\Omega \\
 R_B &= R_1 // R_2 \\
 &= \frac{R_1 R_2}{R_1 + R_2} \\
 &= \frac{27 \times 15}{27 + 15} \\
 &= 9.64 \text{ k}\Omega
 \end{aligned}$$

I_E is then:

$$\begin{aligned}
 I_E &= \frac{3.21 - 0.7}{1.2 + \frac{9.64}{101}} \\
 &= 1.94 \text{ mA}
 \end{aligned}$$

We also have:

$$\begin{aligned}
 g_m &= \frac{I_C}{V_T} \\
 &= \frac{\alpha I_E}{V_T}
 \end{aligned}$$

$$\begin{aligned}
 &= 1.3 \text{ k}\Omega \\
 &= \frac{0.99 \times 1.94}{0.025} \\
 &= 76.8 \text{ mA/V} \\
 &= 1.3 \text{ k}\Omega \\
 r_{\pi} &= \frac{\beta}{g_m} \\
 &= \frac{100}{76.8} \\
 &= 1.3 \text{ k}\Omega \\
 r_o &= \frac{V_A}{I_C} \\
 &= \frac{100}{0.99 \times 1.94} \\
 &= 52.1 \text{ k}\Omega
 \end{aligned}$$

Figure (4.6) shows the equivalent circuit with the input and output resistances. Comparing Figure (4.5) and Figure (4.6), we get:

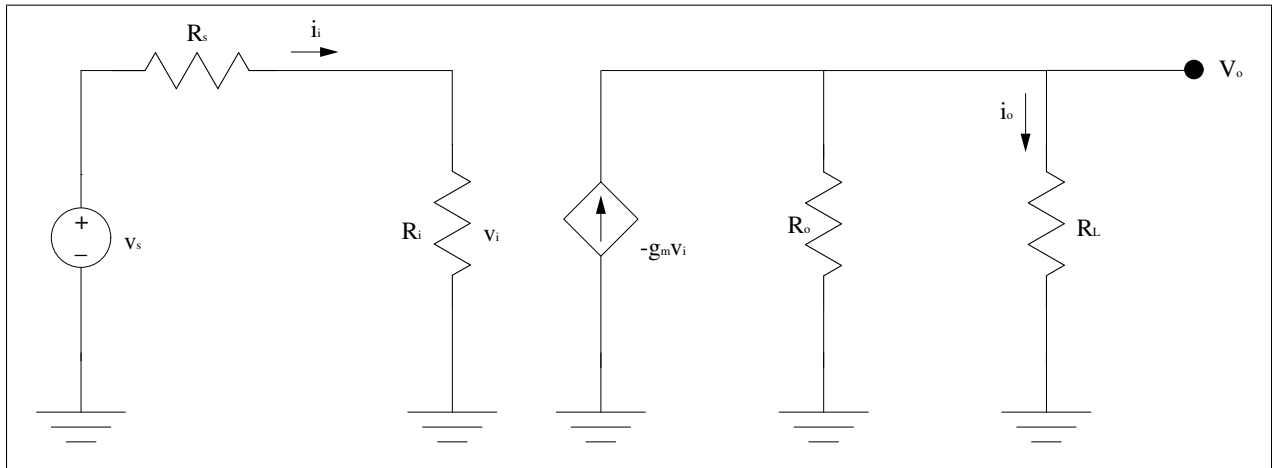


Figure 4.6:

$$\begin{aligned}
 R_i &= R/r_{\pi} \\
 &= 9.64/1.3 \\
 &= 1.15 \text{ k}\Omega \\
 R_o &= R_C/r_o \\
 &= 2.2/52.1 \\
 &= 2.11 \text{ k}\Omega
 \end{aligned}$$

The voltage gain is given by:

$$\begin{aligned}A_v &= \frac{v_o}{v_s} \\&= \frac{v_i}{v_s} \times \frac{v_o}{v_i} \\v_i &= \frac{R_i}{R_s + R_i} \times v_s \\v_o &= -g_m v_i \times (R_o // R_L) \\A_v &= -\frac{R_i}{R_i + R_s} \times g_m \times (R_o // R_L) \\&= -\frac{1.15}{10 + 1.15} \times 76.8 \times (2.11 // 2) \\&= -8.13 \\i_o &= \frac{v_o}{R_L} \\i_i &= \frac{v_s}{R_s + R_i} \\A_i &= \frac{i_o}{i_i} \\&= \frac{v_o}{v_s} \times \frac{R_s + R_i}{R_L} \\&= A_v \times \frac{R_s + R_i}{R_L} \\&= -8.13 \times \frac{10 + 1.15}{2} \\&= -45.3\end{aligned}$$

4.6 Problem 4.91

For the emitter follower circuit shown in Figure (4.7) the BJT used is specified to have β values in the range of 20 to 200 (a distressing situation for the circuit designer). For two extreme values of β ($\beta = 20$ and $\beta = 200$), find:

- I_E , V_E , and V_B ,
- The input resistance R_i ,
- The voltage gain v_o/v_s ,

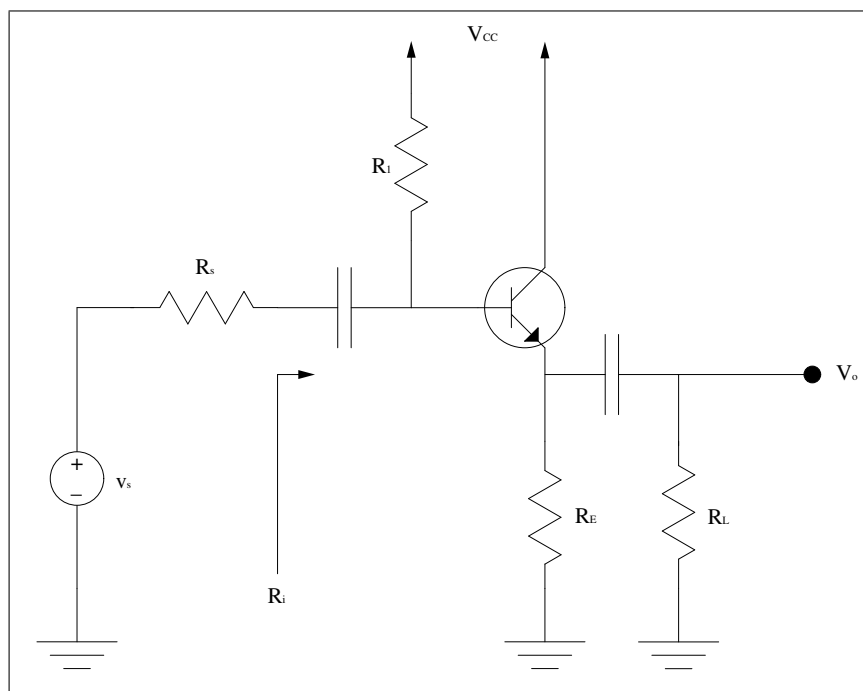


Figure 4.7: In the circuit $V_{CC} = 9\text{ V}$, $R_s = 10\text{ k}\Omega$, $R_1 = 100\text{ k}\Omega$, $R_E = R_L = 1\text{ k}\Omega$. The capacitors are very large.

Solution

- The emitter current I_E , emitter voltage V_E and base voltage V_B are given by:

$$I_E = \frac{V_{CC} - V_{BE}}{R_E + \frac{R_1}{\beta + 1}}$$

$$\begin{aligned}
V_E &= I_E R_E \\
V_B &= V_E + V_{BE} \\
I_{E20} &= \frac{9 - 0.7}{1 + \frac{100}{21}} \\
&= 1.44 \text{ mA} \\
V_{E20} &= 1.44 \times 1 \\
&= 1.44 \text{ V} \\
V_{B20} &= 1.44 + 0.7 \\
I_{E200} &= \frac{9 - 0.7}{1 + \frac{100}{201}} \\
&= 5.54 \text{ mA} \\
V_{E200} &= 5.54 \times 1 \\
&= 5.54 \text{ V} \\
V_{B200} &= 5.54 + 0.7 \\
&= 6.24 \text{ V}
\end{aligned}$$

- (b) To find the input resistance R_i we use the T-model equivalent circuit shown in Figure (4.8). R_i is given by:

$$R_i = R_1 // R'_i$$

and R'_i is defined by:

$$R'_i = \frac{v_b}{i_b}$$

where v_b and i_b are the base voltage and current respectively. The base voltage is defined by:

$$\begin{aligned}
v_b &= i_e \times [r_e + (R_E // R_L)] \\
&= (1 + \beta) \times i_b \times [r_e + (R_E // R_L)] \\
R'_i &= \frac{(1 + \beta) \times i_b \times [r_e + (R_E // R_L)]}{i_b} \\
R_i &= R_1 // (1 + \beta) \times [r_e + (R_E // R_L)] \\
&= 100 // (1 + \beta) \times [r_e + (R_E // R_L)] \\
r_e &= \frac{V_T}{I_E} \\
&= \frac{0.025}{I_E} \\
R_i &= 100 // (1 + \beta) \times \left[\frac{0.025}{I_E} + (R_E // R_L) \right]
\end{aligned}$$

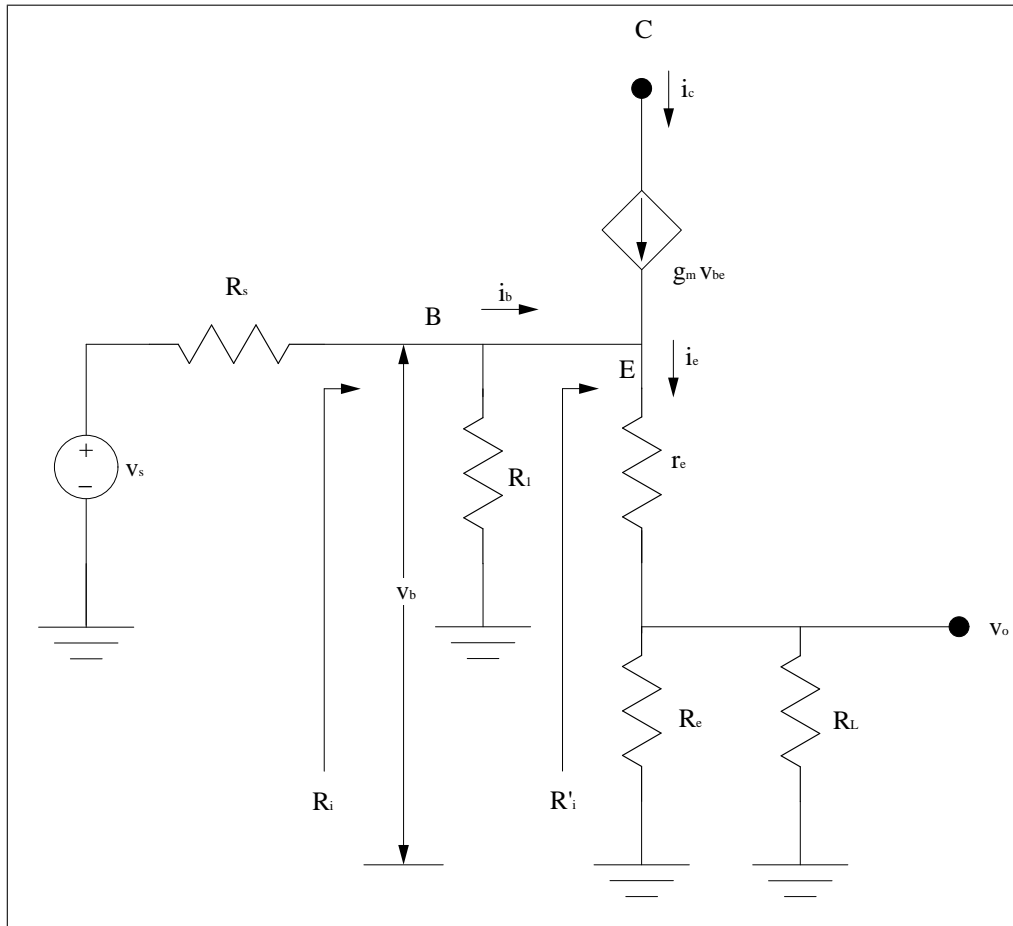


Figure 4.8:

$$\begin{aligned}
 R_{i20} &= 100 // (1 + 20) \times \left[\frac{0.025}{I_{E20}} + (R_E // R_L) \right] \\
 &= 100 // 21 \times \left[\frac{0.025}{1.44} + (1 // 1) \right] \\
 &= 100 // 21 \times (0.0174 + 0.5) \\
 &= 100 // 10.87 \\
 &= 9.8 \text{ k}\Omega
 \end{aligned}$$

$$\begin{aligned}
 R_{i200} &= 100 // (1 + 200) \times \left[\frac{0.025}{I_{E200}} + (R_E // R_L) \right] \\
 &= 100 // 21 \times \left[\frac{0.025}{5.54} + (1 // 1) \right] \\
 &= 100 // 201 \times (0.0045 + 0.5) \\
 &= 100 // 101.4 \\
 &= 50.3 \text{ k}\Omega
 \end{aligned}$$

(c) The voltage gain v_o/v_s can be written as:

$$\frac{v_o}{v_s} = \frac{v_b}{v_s} \times \frac{v_o}{v_b}$$

Using Figure (4.8), we can see that at the input v_s , R_s , and R_i form a series voltage divider with v_b the voltage across R_i we then get:

$$\begin{aligned} v_b &= \frac{R_i}{R_i + R_s} \times v_s \\ \frac{v_b}{v_s} &= \frac{R_i}{R_i + R_s} \end{aligned}$$

while on the output we can see that v_b , r_e , and $R_E//R_L$ form another series voltage divider where v_o is the voltage across $R_E//R_L$, we then get:

$$\begin{aligned} v_o &= \frac{R_E//R_L}{r_e + (R_E//R_L)} \times v_b \\ \frac{v_o}{v_b} &= \frac{R_E//R_L}{r_e + (R_E//R_L)} \\ &= \frac{R_E//R_L}{\frac{V_T}{I_E} + (R_E//R_L)} \end{aligned}$$

The voltage gain is then:

$$\frac{v_o}{v_s} = \frac{R_i}{R_i + R_s} \times \frac{R_E//R_L}{\frac{V_T}{I_E} + (R_E//R_L)}$$

For $\beta = 20$, we get:

$$\begin{aligned} \frac{v_o}{v_s} &= \frac{9.8}{9.8 + 10} \times \frac{0.5}{\frac{0.025}{1.44} + 0.5} \\ &= 0.478 \end{aligned}$$

and for $\beta = 200$:

$$\begin{aligned} \frac{v_o}{v_s} &= \frac{50.3}{50.3 + 10} \times \frac{0.5}{\frac{0.025}{5.54} + 0.5} \\ &= 0.827 \end{aligned}$$